

XOR logic through Arduino

B.Sai Sindhu

CONTENTS

1	Abstract	1
2	Components	1
3	Procedure	2

1 ABSTRACT

In the circuit X and Y are digital inputs, Z is digital output. The equivalent circuit is the logic implementation of XOR Gate.

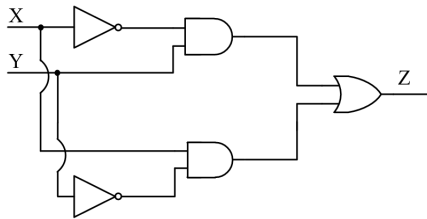


Fig. 1: $Z = X!Y + !XY$

2 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

TABLE I

The figure given below is the pin diagram of Seven Segment Display

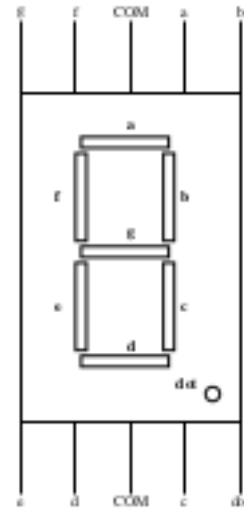


Fig. 2: Seven segment display

The table given below is the connections between 7447 BCD Decoder and Seven Segment Display

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 3

The diagram below shows the pin diagram of 7447 BCD Decoder. The output pins of 7447 are connected to Seven Segment Display using fig 3.

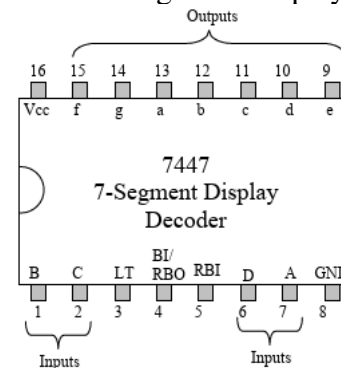


Fig. 4

3 PROCEDURE

1. connect the circuit using 7447 BCD-Seven segment display decoder and Arduino
2. connect the seven segment pins to 7447 using fig 3.
3. connect the input pins X,Y to 0 and 1.
4. connect the output pins of 7447 to Gnd except pin A to D2.
5. change the input pins according to XOR logic and verify the output.
6. Verify the XOR operation in Arduino using the following code and making pin connections according to fig 2,3.

Observe the circuit and verify the program by executing the link provided below.

<https://github.com/sindhu023/FWC/>