

Assignmet 1 : XOR logic Implementation

B.Sai Sindhu

CONTENTS

1	Abstract	1
2	Components	1
3	Procedure	1

1 ABSTRACT

In the circuit X and Y are digital inputs, Z is digital output. The equivalent circuit is the logic implementation of XOR Gate.

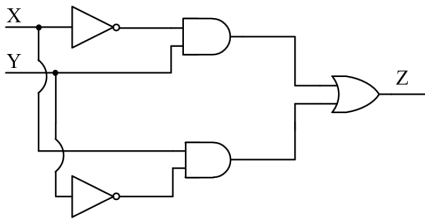


Fig. 1: $Z = X!Y + !XY$

2 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

TABLE I

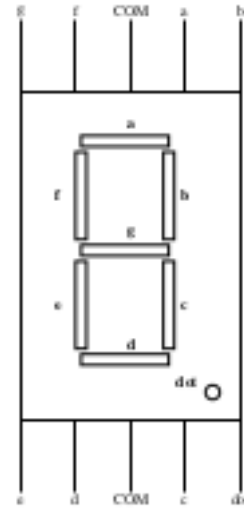


Fig. 2: Seven segment display

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 3

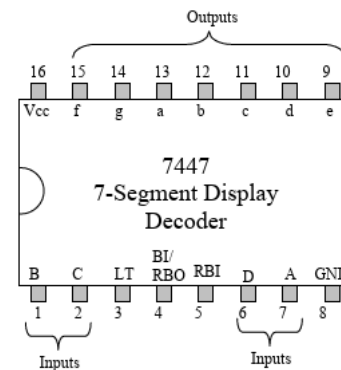


Fig. 4

3 PROCEDURE

1. Connect the circuit as inputs to 0 and 1
2. Connect A pin of 7447 to D2.
3. Connect B,C and D pins of 7447 to GND.
4. Vary the D5 and D6 and observe the output accordingly in the seven segment display.

Observe the circuit by executing the link provided below.

<https://github.com/sindhu023/FWC/ide>