

XOR logic through AVR-GCC

B.Sai Sindhu

CONTENTS

1	Abstract	1
2	Components	1
3	Procedure	2

1 ABSTRACT

Abstract—This manual shows how to implement XOR logic through AVR-GCC.

In the circuit X and Y are digital inputs, Z is digital output. The equivalent circuit is the logic implementation of XOR Gate.

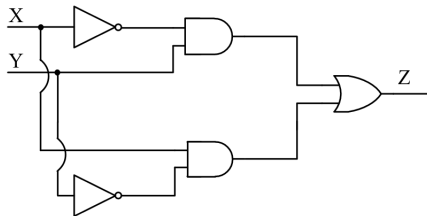


Fig. 1: $Z = X!Y + !XY$

2 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

TABLE I

1. The figure given below is the pin diagram of Seven Segment Display.

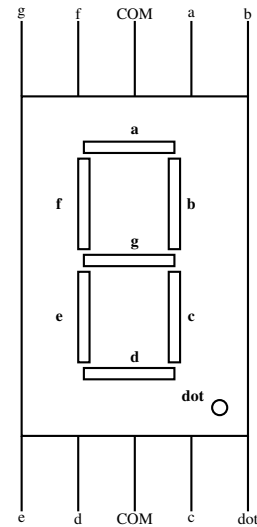


Fig. 2

2. The table given below is the connections between 7447 BCD Decoder and Seven Segment Display

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

TABLE II

3. The diagram below shows the pin diagram of 7447 BCD Decoder. The output pins of 7447 are connected to Seven Segment Display using Table 2.

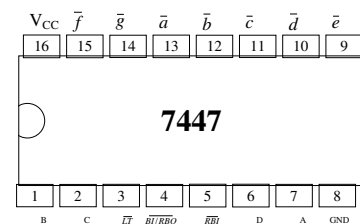


Fig. 3

3 PROCEDURE

1. connect the circuit using 7447 BCD-Seven segment display decoder and Arduino
2. connect the seven segment pins to 7447 using Table 2.
3. connect pin A of 7447 to D2 of Arduino and connect remaining pins B,C and D to GND.
4. connect pins 8,9 of Arduino to Vcc(high) and change to GND(low) simultaneously.
5. Verify the XOR operation in AVR-GCC using the following code and making pin connections according to fig 2,3 and Table 2.

Observe the circuit and verify the program by executing the link provided below.

<https://github.com/sindhu023/FWC/>